
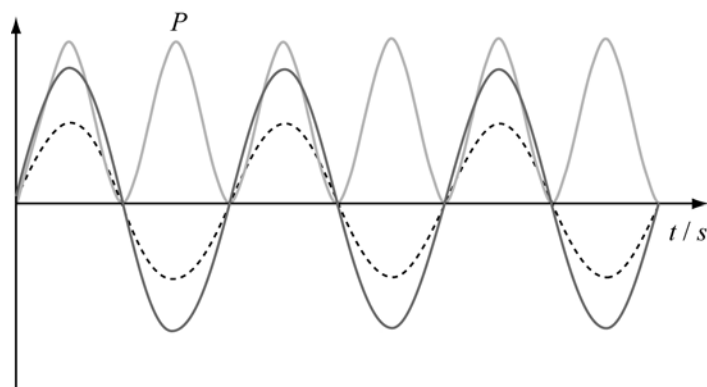


28 Marking scheme: Worksheet (A2)

- 1 a $T = \frac{1}{f}$ [1]
 0.1 s [1]
 b i $t = 0, 0.05 \text{ and } 0.15$ [1]
 ii $t = \frac{1}{4}$ of a period [1]
 $t = 0.025 \text{ s}$ [1]
 iii $t = 0.075 \text{ s}$ [1]
 iv $t = \frac{1}{\sqrt{2}} = \sin(20\pi t)$ [1]
 $t = 0.0125 \text{ s}$ [1]
- 2 a Corresponding parts of each wave occur at the same time. [1]
 b Power P always positive. [1]
 Two peaks for P in time taken for one peak of I and V . [1]
 Sinusoidal shape above axis. [1]

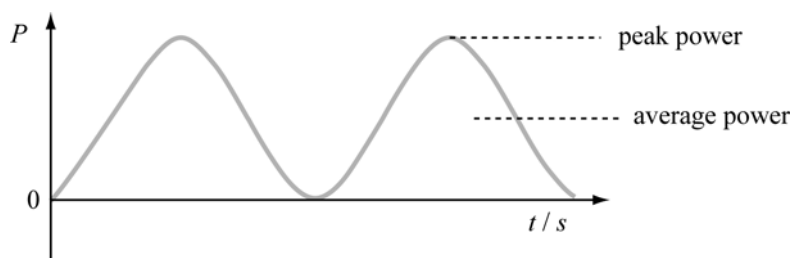

- 3 a i $I = \frac{P}{V} = \frac{690}{230}$ [1]
 $I_{\text{rms}} = 3.0 \text{ A}$ [1]
 ii $I_{\text{peak}} = 3\sqrt{2} = 4.2 \text{ A}$ [1]
 iii $V_{\text{peak}} = 230\sqrt{2} = 325 \text{ V}$ [1]
 b Correct shape all above axis. [1]
 Two cycles shown (i.e. one cycle of current waveform). [1]
 Peak and average power marked. [1]



- 4 a** a.c. [1]
Current is positive and negative OR current flows one way, then the opposite way. [1]
- b** Voltage switches between +2 and -2 V. Power is $\frac{V^2}{R}$, so it has the same value for both positive and negative values of the voltage. [1]
- c** **i** 2 V [1]
ii 2 V [1]
- 5** Average power = $\left(\frac{2.5}{\sqrt{2}}\right) \times \left(\frac{6}{\sqrt{2}}\right)$ [1]
= 7.5 W [1]
- 6 a i** Period = 80 ms = 0.080 s [1]
 $f = \frac{1}{T} = 12.5 \text{ Hz}$ [1]
ii Peak voltage = 4.5 V [1]
r.m.s. voltage = $\frac{4.5}{\sqrt{2}} = 3.2 \text{ V}$ [1]
- b** $V_0 = 4.5 \text{ V}$ [1]
 $\omega = 2\pi f = 2\pi \times 12.5 = 78.5 \text{ s}^{-1} \approx 79 \text{ s}^{-1}$ [1]
- 7 a** $I = \frac{P}{V} = \frac{24}{6}$ [1]
 $I = 4.0 \text{ A}$ [1]
- b** $V_p = 6 \times \frac{1150}{30}$ [1]
 $V_p = 230 \text{ V}$ [1]
- c** $I_p = \frac{24}{230}$ or $I_p = \frac{30 \times 4}{1150}$ [1]
 $I_p = 0.10 \text{ A}$ [1]
- d** Maximum p.d. = $6\sqrt{2}$ [1]
maximum p.d. = 8.5 V [1]
- e** Heat is still produced inside the wires even if it cannot be conducted to the outside. The wires may melt if they cannot lose the heat. [1]
- 8 a** Number of turns on the primary = $\frac{115}{230} \times 500 = 1000$ turns [1]
- b** $I_s = \frac{V_s}{R} = \frac{115}{5000} = 0.023 \text{ A r.m.s.}$ [1]
- c** $I_p = 0.023 \times \frac{500}{1000} = 0.0125 \text{ A} \approx 0.013 \text{ A r.m.s.}$ [1]
- d** Peak voltage = $115\sqrt{2} = 162 \text{ V}$ [1]
so the cables will break down. [1]
- 9 a** $I = \frac{P}{V} = \frac{1000}{100} = 10 \text{ A r.m.s.}$ [1]
 $P = I^2 R = 10^2 \times 5 = 500 \text{ W}$ [1]
- b** At high voltages the current is less for the same power. [1]
Power lost in cable = $I^2 R$ so power lost is less. [1]