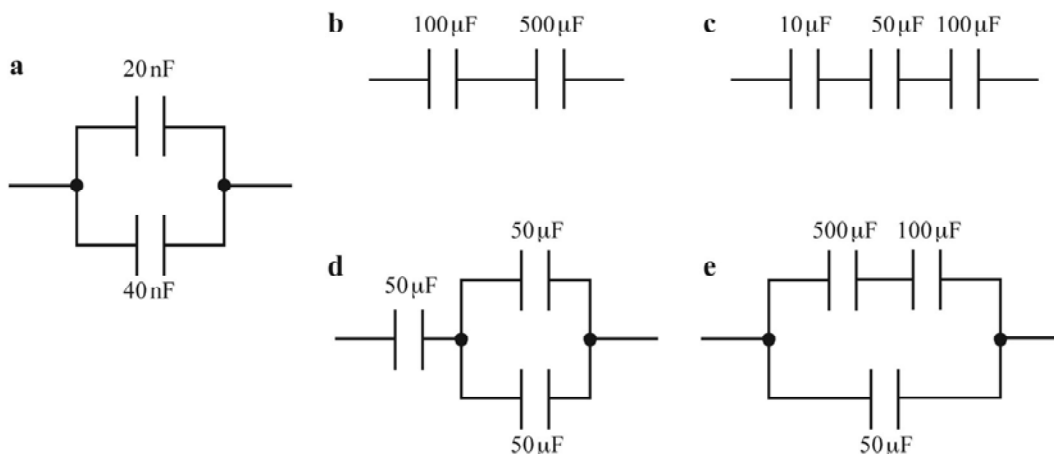



24 Worksheet (A2)

Data needed to answer questions can be found in the Data, formulae and relationships sheet.

- 1 A $30\ \mu\text{F}$ capacitor is connected to a $9.0\ \text{V}$ battery.
 - a Calculate the charge on the capacitor. [2]
 - b How many excess electrons are there on the negative plate of the capacitor? [2]
- 2 The p.d. across a capacitor is $3.0\ \text{V}$ and the charge on the capacitor is $150\ \text{nC}$.
 - a Determine the charge on the capacitor when the p.d. is:
 - i $6.0\ \text{V}$ [2]
 - ii $9.0\ \text{V}$. [2]
 - b Calculate the capacitance of the capacitor. [2]
- 3 A $1000\ \mu\text{F}$ capacitor is charged to a potential difference of $9.0\ \text{V}$.
 - a Calculate the energy stored by the capacitor. [2]
 - b Determine the energy stored by the capacitor when the p.d. across it is doubled. [2]
- 4 For each circuit below, determine the total capacitance of the circuit. [13]




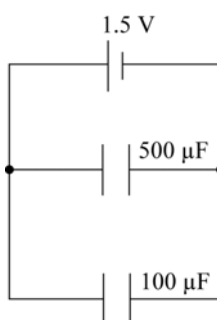- 5 The diagram shows an electrical circuit.




- a Calculate the total capacitance of the two capacitors in parallel. [2]
- b What is the potential difference across each capacitor? [1]
- c Calculate the total charge stored by the circuit. [2]
- d Calculate the total energy stored by the capacitors. [2]

- 6** A $10\,000\ \mu\text{F}$ capacitor is charged to its maximum operating voltage of $32\ \text{V}$. The charged capacitor is discharged through a filament lamp. The flash of light from the lamp lasts for $300\ \text{ms}$.
- Calculate the energy stored by the capacitor. [2]
 - Determine the average power dissipated in the filament lamp. [2]
- 7** The diagram shows a $1000\ \mu\text{F}$ capacitor charged to a p.d. of $12\ \text{V}$.
- Calculate the charge on the $1000\ \mu\text{F}$ capacitor. [2]

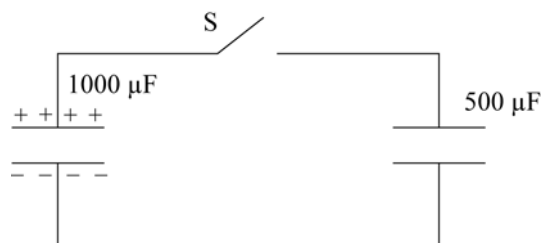


- The $1000\ \mu\text{F}$ capacitor is connected across an uncharged $500\ \mu\text{F}$ capacitor by closing the switch **S**. The charge initially stored by the $1000\ \mu\text{F}$ capacitor is now shared with the $500\ \mu\text{F}$ capacitor.
 - Calculate the total capacitance of the capacitors in parallel. [2]
 - Show that the p.d. across each capacitor is $8.0\ \text{V}$. [2]
- 8** The diagram shows a circuit used to measure the capacitance of a capacitor.

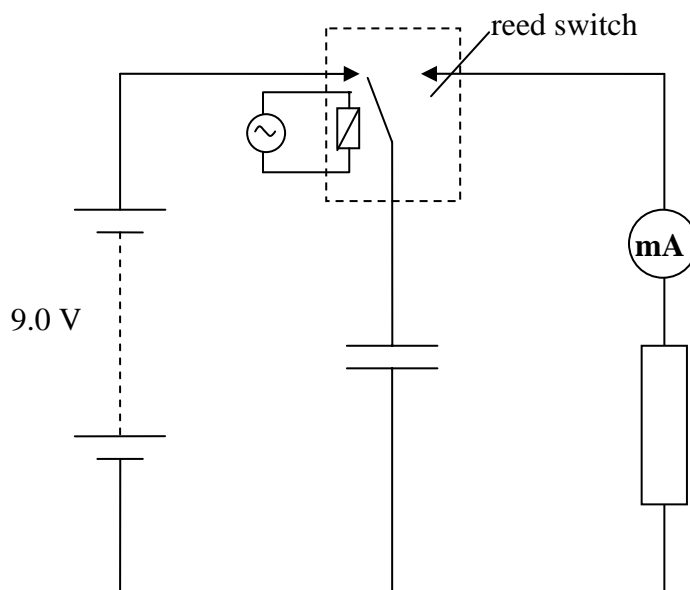

The reed switch vibrates between the two contacts with a frequency of $50\ \text{Hz}$. On each oscillation the capacitor is fully charged and totally discharged. The current through the milliammeter is $225\ \text{mA}$.

- Calculate the charge that flows off the capacitor each time it is discharged. [1]
- Calculate the capacitance of the capacitor. [2]
- Calculate the current through the milliammeter when a second identical capacitor is connected:
 - in parallel with the original capacitor [1]
 - in series with the original capacitor. [1]

- 9** A capacitor of capacitance $200\ \mu\text{F}$ is connected across a $200\ \text{V}$ supply.
- a** Calculate the charge stored on the plates. [1]
 - b** Calculate the energy stored on the capacitor. [1]
- The capacitor is now disconnected from the power supply and is connected across a $100\ \mu\text{F}$ capacitor.
- c** Calculate the potential difference across the capacitors. [3]
 - d** Calculate the total energy stored on the capacitors. [2]
 - e** Suggest where the energy has been lost. [1]
- 10** The diagram below shows a charged capacitor of capacitance C . When the switch S is closed, this capacitor is connected across the uncharged capacitor of capacitance $2C$. Calculate the percentage of energy lost as heat in the resistor and explain why the actual resistance of the resistor is irrelevant. [7]

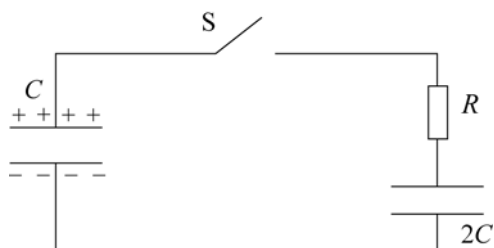

Total: _____
64

Score: _____ %